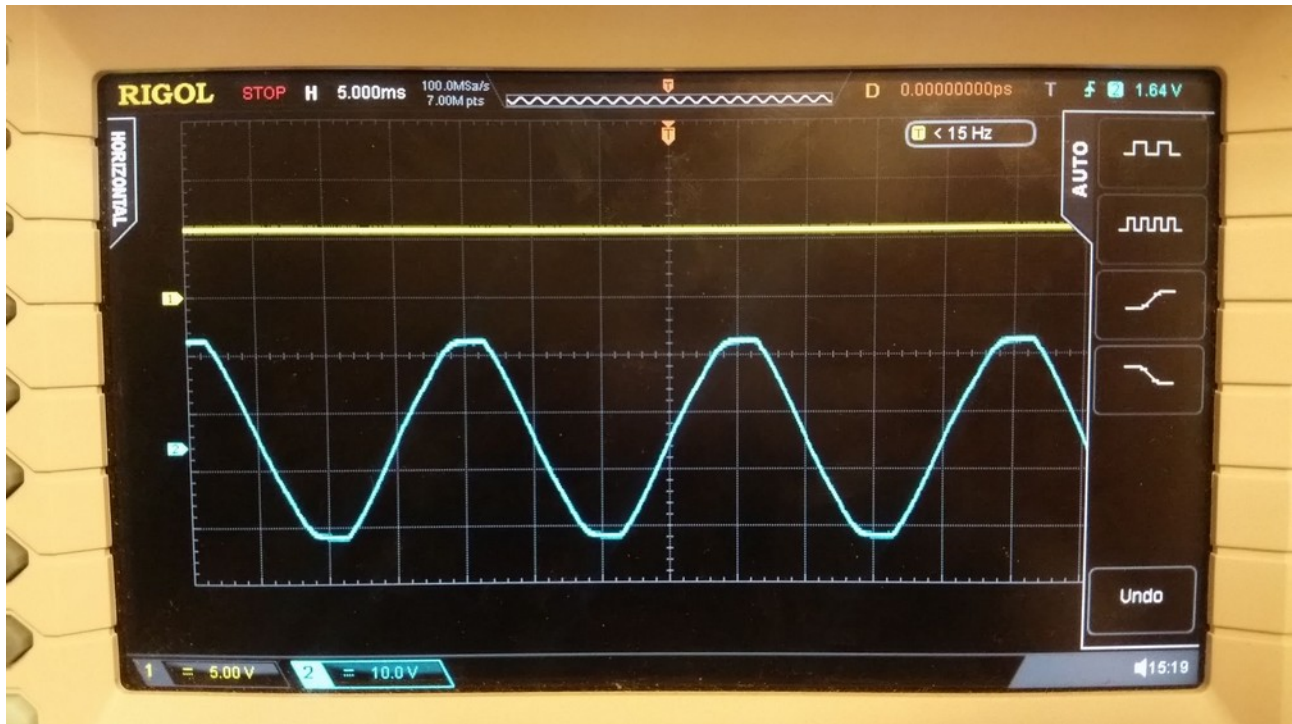



BIAS input / output

Following done while a single VT is connected.

VT input at the connector pad:




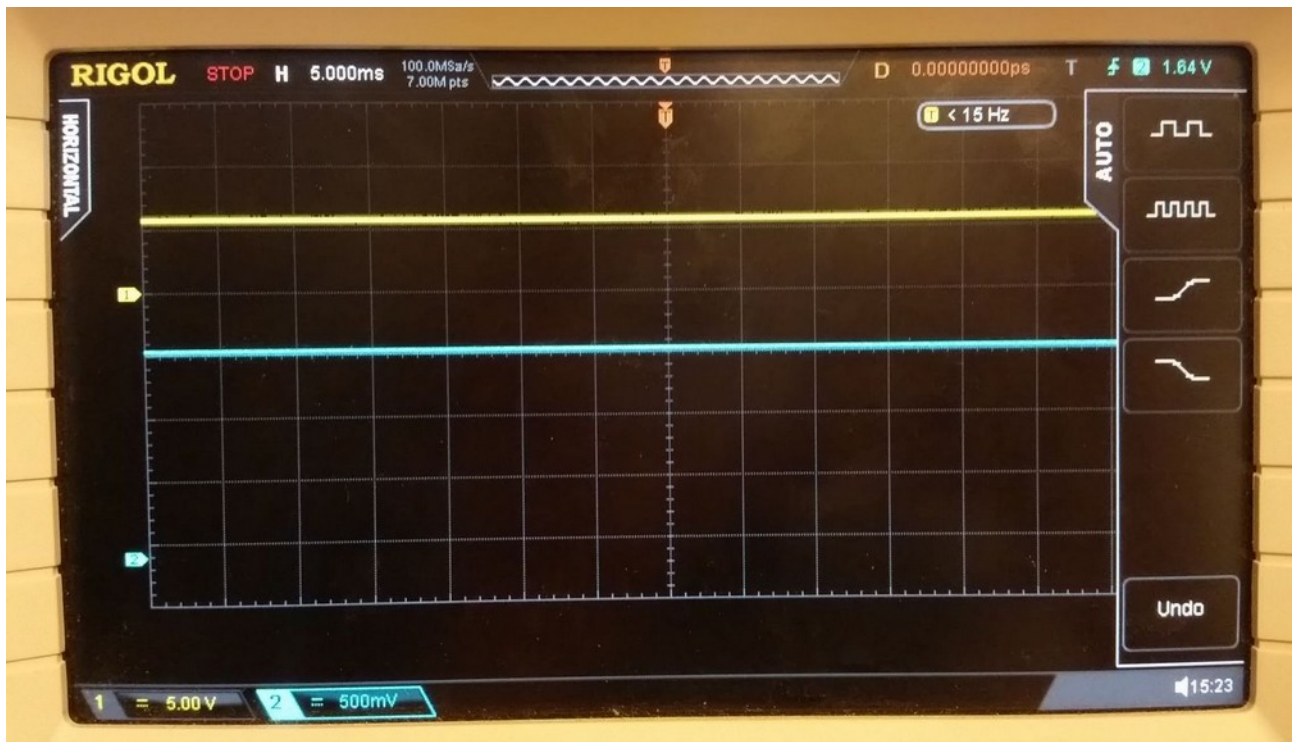The following shows the 5V input in Yellow, Bias output in Blue, probed at the VT connection.



Zoomed in:

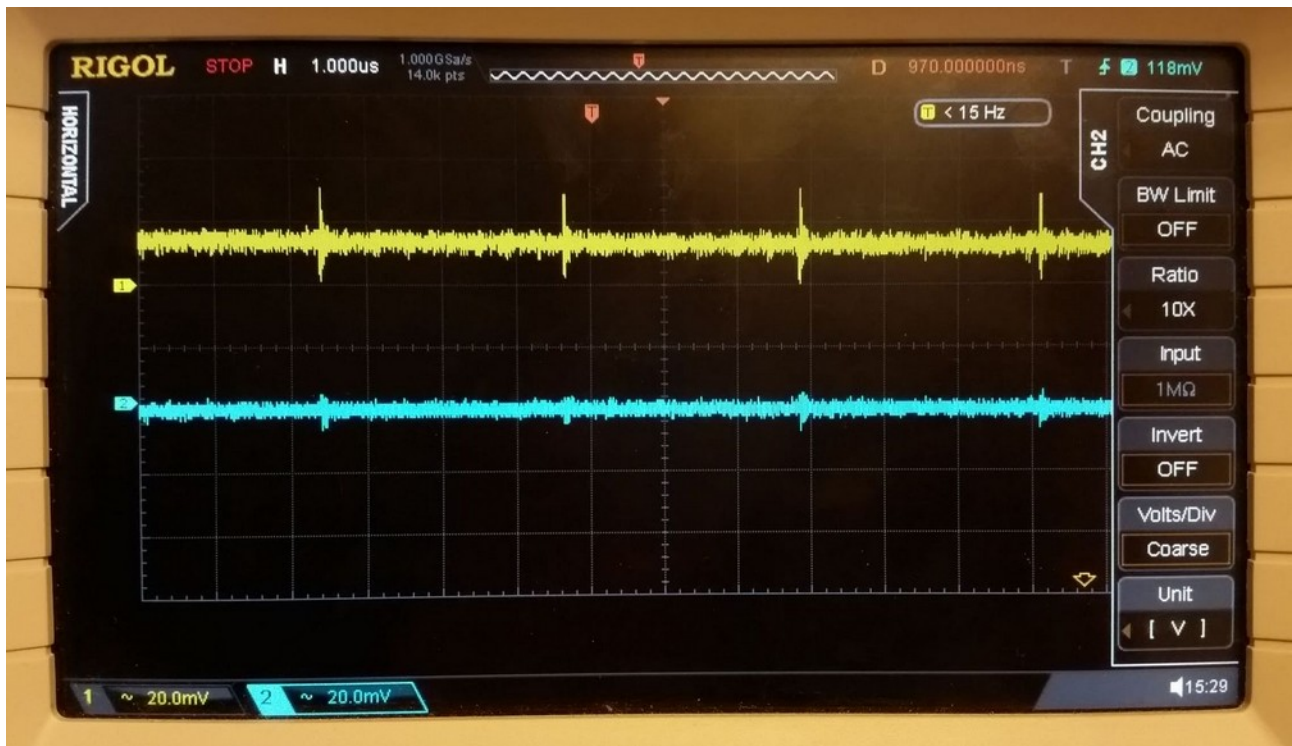BIAS output with 2.2uF capacitor on it's 10k/10k input:



BIAS output with no filtering capacitor on it's input.

